


$$R_1 = \frac{6 \cdot 6}{6 + 6} = \frac{36}{12} = 3 \Omega$$

$$R_4 = \frac{3 \cdot 6 \cdot 6}{6 + 3 \cdot 6} = 2.25$$

$$R_2 = 3 + 6 = 9 \Omega$$

$$R_3 = \frac{6 \cdot 9}{6 + 9} = \frac{54}{15} = 3.6 \Omega$$
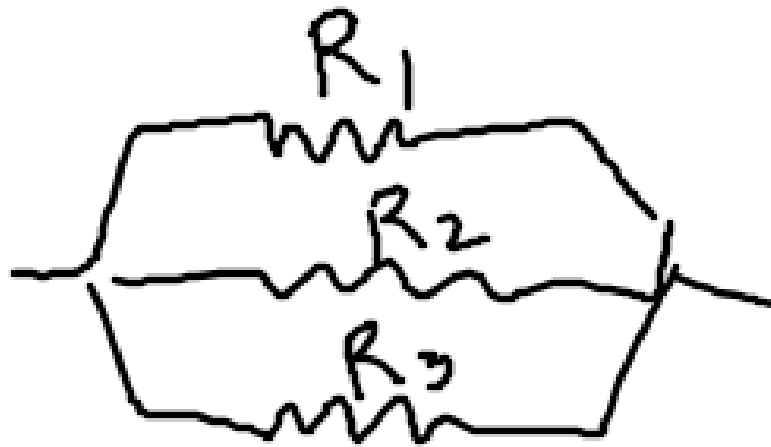
$$R_T = R_4 + 6 = 2.25 + 6 = \underline{\underline{8.25 \Omega}}$$



$$R = \frac{R \cdot R_2}{R_1 + R_2}$$

↓

$$\underline{2R}$$

$$\frac{1}{R_{||}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{||}} = \frac{R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2}{R_1 \cdot R_2 \cdot R_3}$$

$$R_{||} = \frac{R_1 \cdot R_2 \cdot R_3}{R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2}$$

$$3) \quad \boxed{q_e = 16 \cdot 10^{-19} \text{ C}}$$

$$I = 1 \text{ A} \quad t = 1 \text{ s}$$

$$\frac{\text{Ohm}}{V = I \cdot R}$$

$$I = \frac{q}{t}$$

$$1 = \frac{q}{1}$$

$$q = 1 \text{ C}$$

R3

$$1e^- \text{ --- } 16 \cdot 10^{-19} \text{ C}$$

$$x \text{ --- } 1 \text{ C}$$

$$x = \frac{1}{16 \cdot 10^{-19}} = \frac{625 \cdot 10^{18}}{e/s}$$

$$6) V = IR$$

$$30 = I \cdot 20$$

$$I = \frac{30}{20}$$

$$I = 1.5 \text{ A}$$

7] $R = 100 \Omega$ $\xrightarrow{10^{-3}}$ $\overbrace{3 \cdot 10^{-4}}$

$$I = 0.3 \text{ mA} = 3 \cdot 10^{-4}$$


$\frac{0.3}{1000} = 0.0003$

$$V = IR$$

$$V = 3 \cdot 10^{-4} \cdot 100 = 3 \cdot 10^{-2} = \underline{\underline{0.03 \text{ V}}}$$

8)

$$L = 10 \text{ m}$$

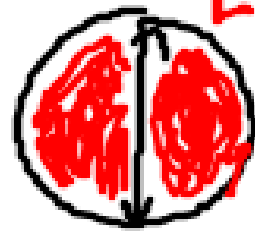

$$S = \pi \cdot r^2 =$$
$$S = 3.14 \left(\frac{5 \cdot 10^{-4}}{2} \right)^2$$

$$\phi = 0.5 \text{ mm} = 0.0005 = 5 \cdot 10^{-4} \text{ m}$$

$$\rho = 1.7 \cdot 10^{-8}$$

$$S = 1.96 \cdot 10^{-7} \text{ m}^2$$

$$R = \rho \frac{L}{S} = 1.7 \cdot 10^{-8} \cdot \frac{10}{1.96 \cdot 10^{-7}} = 0.86 \Omega$$

$$9) R = 100 \Omega$$

$$S = 0.1 \text{ mm}^2 \cdot \frac{1 \text{ m}^2}{10^6 \text{ mm}^2} = 1 \cdot 10^{-7} \text{ m}^2$$

$$\rho = 2.4 \cdot 10^{-8}$$

$$100 = R = \rho \frac{L}{S} = \frac{2.4 \cdot 10^{-8} \cdot L}{10^{-7}}$$

$$L = \frac{100 \cdot 10^{-7}}{2.4 \cdot 10^{-8}} = \underline{\underline{416.7 \text{ m}}}$$

$$10) \quad V = ? \quad I = 2 \text{ A}$$

$$V = IR$$

$$L = 500 \text{ m}$$

$$\phi = 2 \text{ mm} \rightarrow \text{radio} = 1 \text{ mm} = 10^{-3} = 0.001$$

$$R = \rho \cdot \frac{L}{S} = 1.7 \cdot 10^{-8} \cdot \frac{500}{3.14 \cdot 10^{-6}} =$$
$$= 2.7 \Omega$$

$$V = 2 \cdot 2.7 = \underline{\underline{5.4 \text{ V}}}$$

$$S = \pi \cdot r^2 =$$
$$= \pi \cdot 0.001^2 =$$
$$= \underline{\underline{3.14 \cdot 10^{-6} \text{ m}^2}}$$


13 y 24



$$R_1 = \frac{2 \cdot 4}{2+4} = \frac{8}{6} = 1\frac{1}{3} \Omega$$

$$R_2 = 4 + R_1 = 4 + 1\frac{1}{3} = 5\frac{1}{3} \Omega$$
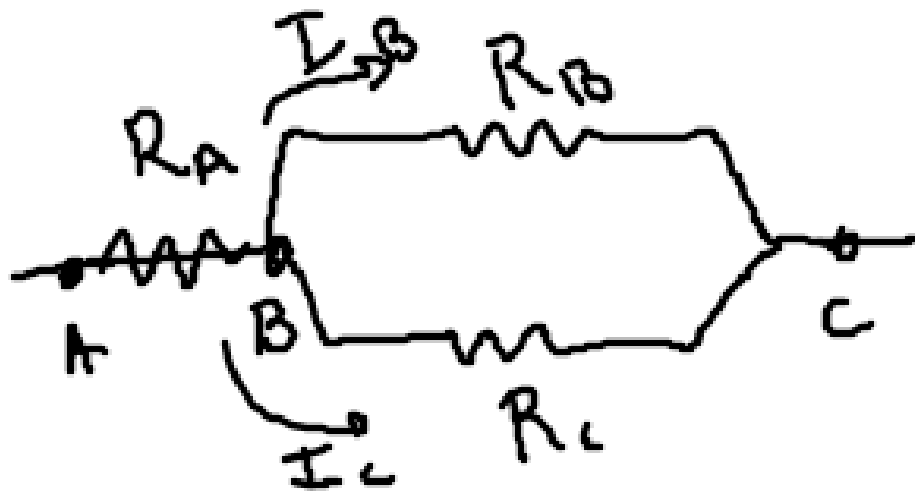
$$V = IR = 3 \cdot 5\frac{1}{3} = \underline{15\frac{1}{3}} \text{ V}$$



$$R_A \rightarrow I = 3\text{ A}$$


$$V_{AB} = I \cdot R = 3 \cdot 4 = 12\text{ V}$$

$$V_{BC} = 15'9 - 12 = 3'9\text{ V}$$


$$I_B \rightarrow V_{BC} = I_B \cdot R_B \rightarrow I_B = \frac{3'9}{2} = 1'9\text{ A}$$

$$I_C \rightarrow V_{BC} = I_C \cdot R_C \rightarrow I_C = \frac{3'9}{4} = 0'9\text{ A}$$

$$R_A = 3 \Omega$$

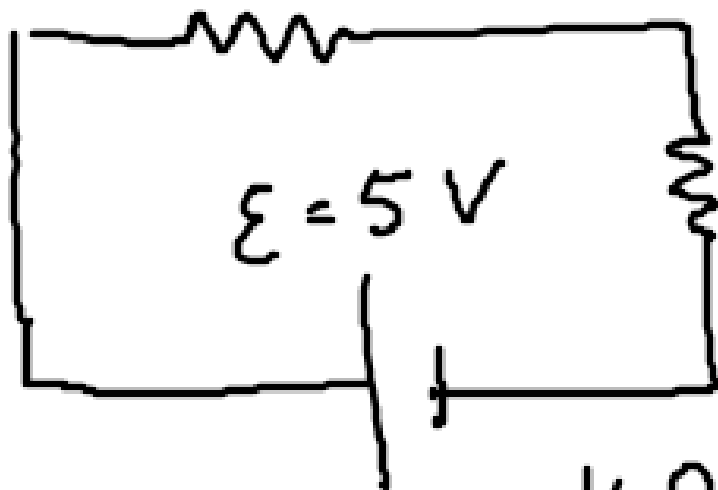


$$R_B = 4 \Omega$$

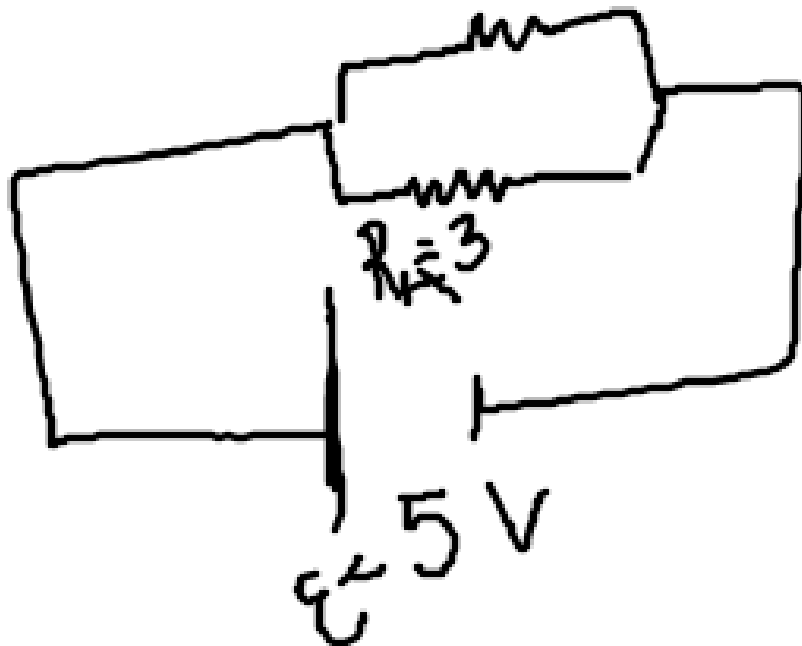

$$\left. \begin{array}{l} V_{R_A} \quad | \quad V_{R_B} \\ I_{R_A} \quad | \quad I_{R_B} \\ I_T \end{array} \right\}$$

$$R_A = 3 \Omega$$

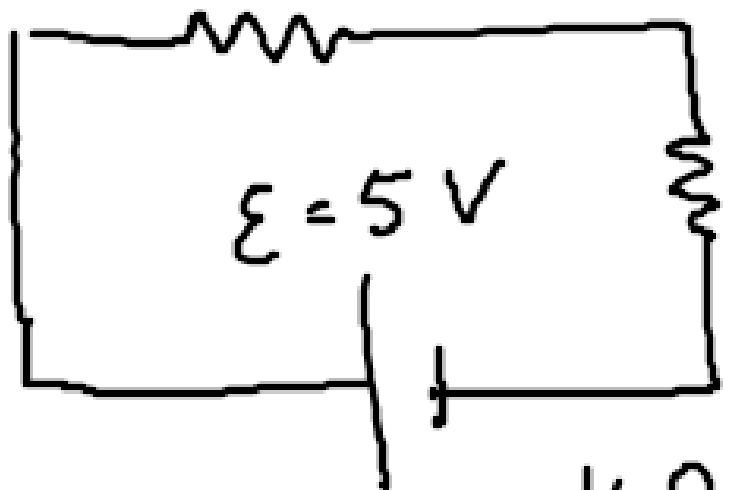

$$R_B = 4 \Omega$$

$$V_T = I_T \cdot R_T$$

$$5 = I_T \cdot 7$$

$$I_T = 0.71 \text{ A}$$


$$R_T = R_A + R_B =$$

$$= 7 \Omega$$

$$4 \Omega = R_1$$

$$V_{RA} = I_{RA} \cdot R_A =$$
$$= 0.71 \cdot 3 = 2.13 \text{ V}$$
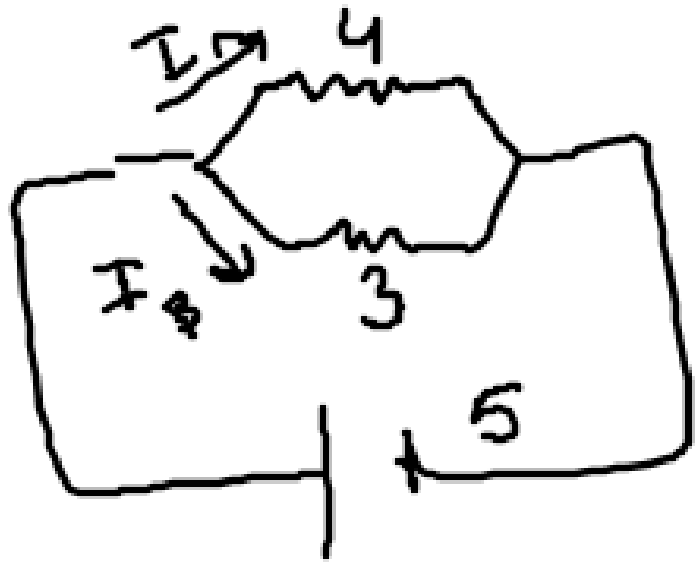
$$V_{RB} = I_{RB} \cdot R_B =$$
$$= 0.71 \cdot 4 = 2.84 \text{ V}$$



$$R_T = \frac{4 \cdot 3}{4 + 3} = 1.7 \Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{5}{1.7} = 2.9 \text{ A}$$

$$I_A = \frac{5}{4} = 1.25 \text{ A} \quad I_B = \frac{5}{3} = 1.66 \text{ A}$$